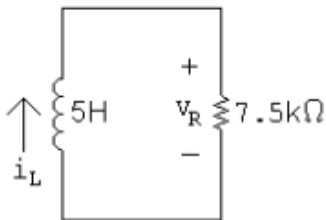


Homwork 4 جواب سوالات

-۲

[a] $t > 0$:

$$L_{\text{eq}} = 1.25 + \frac{60}{16} = 5 \text{ H}$$



$$i_L(t) = i_L(0)e^{-t/\tau} \text{ mA}; \quad i_L(0) = 2 \text{ A}; \quad \frac{1}{\tau} = \frac{R}{L} = \frac{7500}{5} = 1500$$


$$i_L(t) = 2e^{-1500t} \text{ A}, \quad t \geq 0$$

$$v_R(t) = Ri_L(t) = (7500)(2e^{-1500t}) = 15,000e^{-1500t} \text{ V}, \quad t \geq 0^+$$

$$v_o = -3.75 \frac{di_L}{dt} = 11,250e^{-1500t} \text{ V}, \quad t \geq 0^+$$

$$[\text{b}] \quad i_o = \frac{-1}{6} \int_0^t 11,250e^{-1500x} dx + 0 = 1.25e^{-1500t} - 1.25 \text{ A}$$

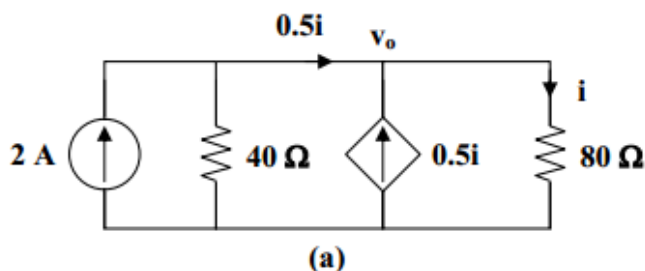Before $t = 0$, the circuit has reached steady state so that the capacitor acts like an open circuit. The circuit is equivalent to that shown in Fig. (a) after transforming the voltage source.




$$0.5i = 2 - \frac{v_o}{40}, \quad i = \frac{v_o}{80}$$

$$\text{Hence, } \frac{1}{2} \frac{v_o}{80} = 2 - \frac{v_o}{40} \longrightarrow v_o = \frac{320}{5} = 64$$


$$i = \frac{v_o}{80} = \underline{\underline{0.8 \text{ A}}}$$

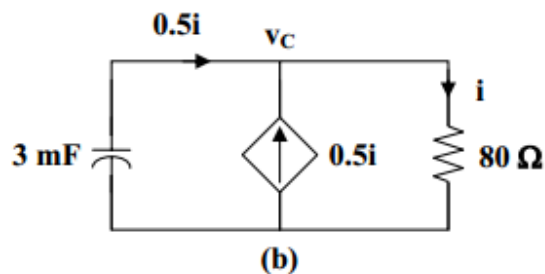After $t = 0$, the circuit is as shown in Fig. (b).



$$v_c(t) = v_c(0)e^{-t/\tau}, \quad \tau = R_{th}C$$

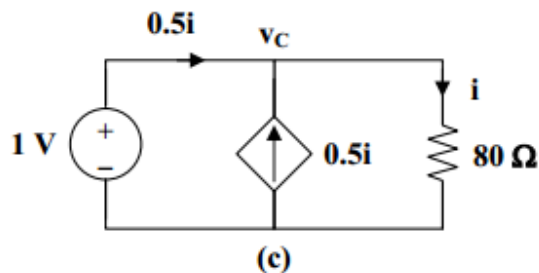To find R_{th} , we replace the capacitor with a 1-V voltage source as shown in Fig. (c).



$$i = \frac{v_c}{80} = \frac{1}{80}, \quad i_o = 0.5i = \frac{0.5}{80}$$


$$R_{th} = \frac{1}{i_o} = \frac{80}{0.5} = 160 \, \Omega, \quad \tau = R_{th}C = 480$$

$$v_c(0) = 64 \, V$$


$$v_c(t) = 64 e^{-t/480}$$

$$0.5i = -i_c = -C \frac{dv_c}{dt} = -3 \left(\frac{1}{480} \right) 64 e^{-t/480}$$
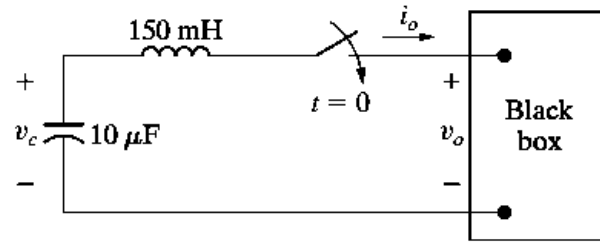
$$i(t) = \underline{0.8 e^{-t/480} u(t) A}$$



$$\begin{aligned}
 v_c &= -\frac{1}{10 \times 10^{-6}} \left(\int_0^t 0.2e^{-800x} dx - \int_0^t 0.04e^{-200x} dx \right) + 5 \\
 &= 25(e^{-800t} - 1) - 20(e^{-200t} - 1) + 5 \\
 &= 25e^{-800t} - 20e^{-200t} \text{ V} \\
 v_L &= 150 \times 10^{-3} \frac{di_o}{dt} \\
 &= 150 \times 10^{-3} (-160e^{-800t} + 8e^{-200t}) \\
 &= -24e^{-800t} + 1.2e^{-200t} \text{ V} \\
 v_o &= v_c - v_L \\
 &= (25e^{-800t} - 20e^{-200t}) - (-24e^{-800t} + 1.2e^{-200t}) \\
 &= 49e^{-800t} - 21.2e^{-200t} \text{ V, } t > 0
 \end{aligned}$$

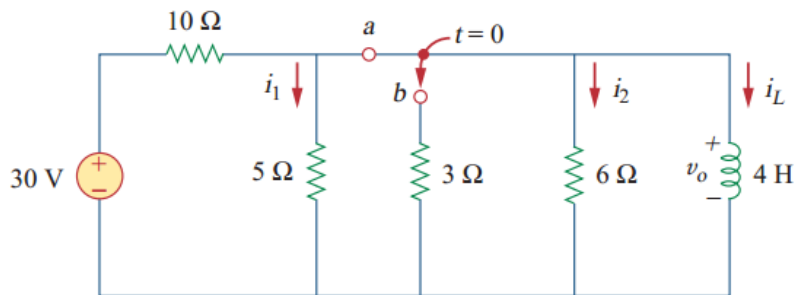

- (a) When the switch is in position A, the 5-ohm and 6-ohm resistors are short-circuited so that

$$\underline{i_1(0) = i_2(0) = v_o(0) = 0}$$

but the current through the 4-H inductor is $i_L(0) = 30/10 = 3\text{A}$.

- (b) When the switch is in position B,

$$R_{Th} = 3 // 6 = 2\Omega, \quad \tau = \frac{L}{R_{Th}} = 4/2 = 2\text{sec}$$


$$i_L(t) = i_L(\infty) + [i_L(0) - i_L(\infty)]e^{-t/\tau} = 0 + 3e^{-t/2} = \underline{3e^{-t/2} \text{ A}}$$

$$(c) \quad i_1(\infty) = \frac{30}{10+5} = \underline{2 \text{ A}}, \quad i_2(\infty) = -\frac{3}{9}i_L(\infty) = \underline{0 \text{ A}}$$

$$v_o(t) = L \frac{di_L}{dt} \longrightarrow \underline{v_o(\infty) = 0 \text{ V}}$$


Note that for $t > 0$, $v_o = (10/15)v_c$, where v_c is the voltage across the 25 nF capacitor. Thus we will find v_c first.

$t < 0$

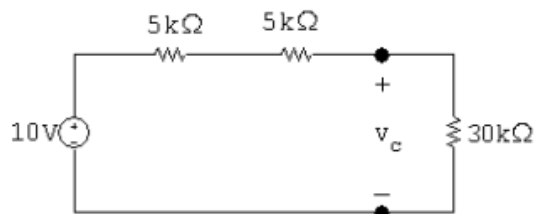

$$v_c(0) = \frac{30}{40}(10) = 7.5 \text{ V}$$

$0 \leq t \leq 0.2 \text{ ms}$:

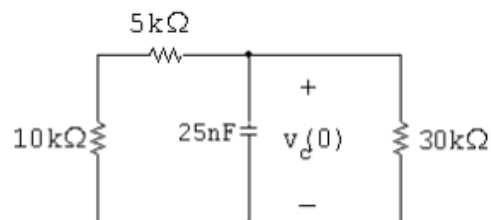


$$\tau = R_e C, \quad R_e = 15,000 \parallel 30,000 = 10 \text{ k}\Omega$$

$$\tau = (10 \times 10^3)(25 \times 10^{-9}) = 0.25 \text{ ms}, \quad \frac{1}{\tau} = 4000$$

$$v_c = 7.5e^{-4000t} \text{ V}, \quad t \geq 0$$

$$v_c(0.2 \text{ ms}) = 7.5e^{-0.8} = 3.37 \text{ V}$$

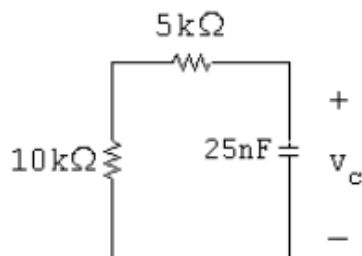
$0.2 \text{ ms} \leq t \leq 0.8 \text{ ms}$:



$$\tau = (15 \times 10^3)(2.5 \times 10^{-9}) = 375 \mu\text{s}, \quad \frac{1}{\tau} = 2666.67$$

$$v_c = 3.37e^{-2666.67(t-200 \times 10^{-6})} \text{ V}$$

$$0.8 \text{ ms} \leq t <:$$

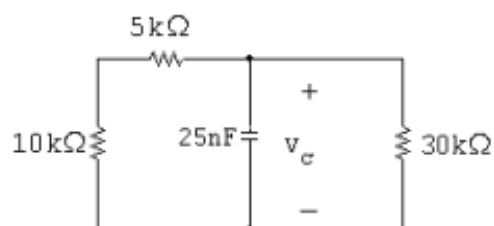

$$\tau = 0.25 \text{ ms}, \quad \frac{1}{\tau} = 4000$$

$$v_c(0.8 \text{ ms}) = 3.37e^{-2666.67(800-200)10^{-6}} = 3.37e^{-1.6} = 0.68 \text{ V}$$


$$v_c = 0.68e^{-4000(t-0.8 \times 10^{-3})} \text{ V}$$

$$v_c(1 \text{ ms}) = 0.68e^{-4000(1-0.8)10^{-3}} = 0.68e^{-0.8} = 0.306 \text{ V}$$

$$v_o = (10/15)(0.306) = 0.204 \text{ V}$$

با توجه به اینکه دو منبع مستقل داریم از صحت آنرا استفاده نمی‌کنیم:


اثر منبع ولتاژ V_s

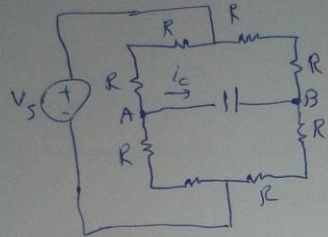


با توجه به اینکه بین دو ترمینال A و B یک ولتاژ داریم و ولتاژ ترمینال A و B برابر بود و جریان i_c برابر هم می‌باشد.
پس ولتاژ V_A تأثیر در جریان i_c نخواهد داشت.

اثر منبع جریان

$$\frac{1}{R} u(t)$$

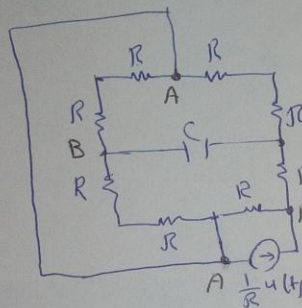

دارد درین حالت

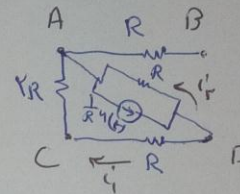

$$V_C(\infty) = V_B - V_C$$

از مقاومت R بین ترمینال A و B جریان نمی‌گذرد پس $\frac{1}{R} u(t)$ بین مقاومت‌های دیگر مدار تقسیم می‌شود:


$$V_A = V_B, \quad i_1 = \frac{R \times (\frac{1}{R} u(t))}{R + R + 2R} = \frac{1}{4R} u(t)$$

$$V_A - V_C = -2R \left(\frac{1}{4R} \right) = -\frac{1}{2}$$

$$V_C(\infty) = -\frac{1}{2}$$

چون قبل از $t=0$ منبع برای شارژ خازن وجود ندارد $V_C(0) = 0$

محاسبه τ : منبع مستقل صفر

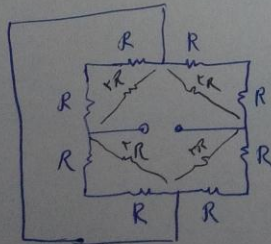

$$R_{eq} = (2R \parallel 2R) + (2R \parallel 2R) = 2R$$

$$\tau = 2RC$$

$$V_C(t) = V_C(\infty) + (V_C(0) - V_C(\infty)) e^{-\frac{t}{\tau}} = -\frac{1}{2} (1 - e^{-\frac{t}{2RC}})$$

$$i_C(t) = C \frac{dV_C(t)}{dt} = C \left(-\frac{1}{2} \times \frac{1}{2RC} \right) e^{-\frac{t}{2RC}} = -\frac{1}{4R} e^{-\frac{t}{2RC}}$$