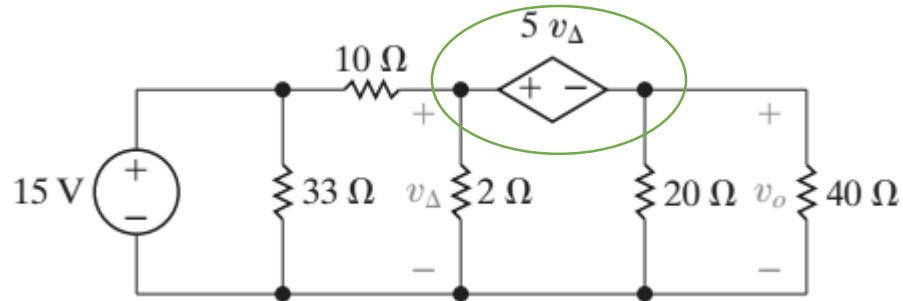


## Homwork 2 جواب سوالات

-۲




Place  $5v_{\Delta}$  inside a supernode and use the lower node as a reference. Then

$$\frac{v_{\Delta} - 15}{10} + \frac{v_{\Delta}}{2} + \frac{v_{\Delta} - 5v_{\Delta}}{20} + \frac{v_{\Delta} - 5v_{\Delta}}{40} = 0$$

$$12v_{\Delta} = 60; \quad v_{\Delta} = 5 \text{ V}$$
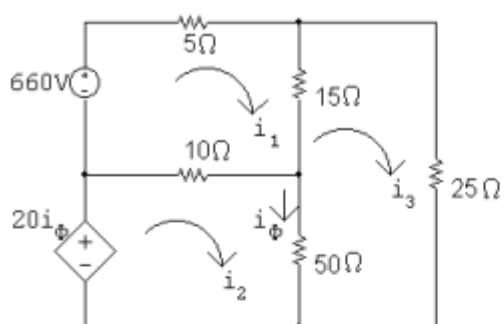
$$v_o = v_{\Delta} - 5v_{\Delta} = -4(5) = -20 \text{ V}$$



$$660 = 30i_1 - 10i_2 - 15i_3$$

$$20i_\phi = -10i_1 + 60i_2 - 50i_3$$


$$0 = -15i_1 - 50i_2 + 90i_3$$

$$i_\phi = i_2 - i_3$$

$$\text{Solving, } i_1 = 42 \text{ A; } i_2 = 27 \text{ A; } i_3 = 22 \text{ A; } i_\phi = 5 \text{ A}$$

$$20i_\phi = 100 \text{ V}$$
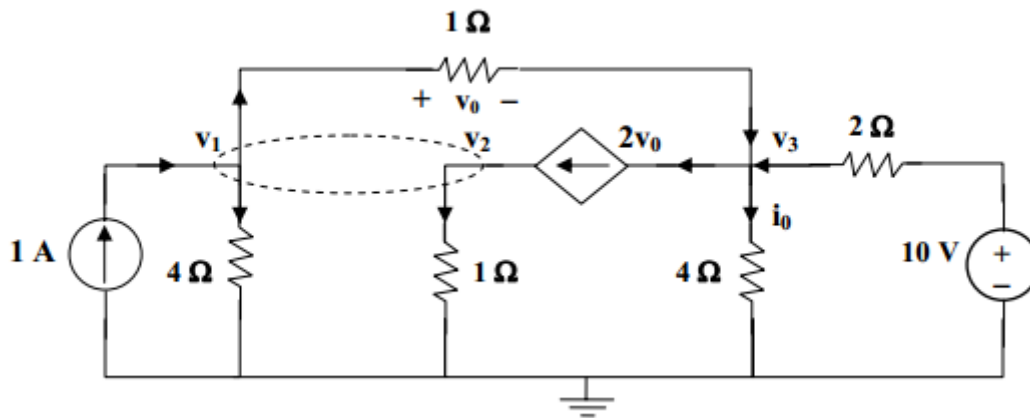
$$p_{20i_\phi} = -100i_2 = -100(27) = -2700 \text{ W}$$



At the supernode,

$$1 + 2v_0 = \frac{v_1}{4} + \frac{v_2}{1} + \frac{v_1 - v_3}{1} \quad (1)$$

But  $v_0 = v_1 - v_3$ . Hence (1) becomes,

$$4 = -3v_1 + 4v_2 + 4v_3 \quad (2)$$

At node 3,

$$2v_0 + \frac{v_3}{4} = v_1 - v_3 + \frac{10 - v_3}{2}$$

or


$$20 = 4v_1 + 0v_2 - v_3 \quad (3)$$

At the supernode,  $v_2 = v_1 + 4i_0$ . But  $i_0 = \frac{v_3}{4}$ . Hence,

$$v_2 = v_1 + v_3 \quad (4)$$

Solving (2) to (4) leads to,
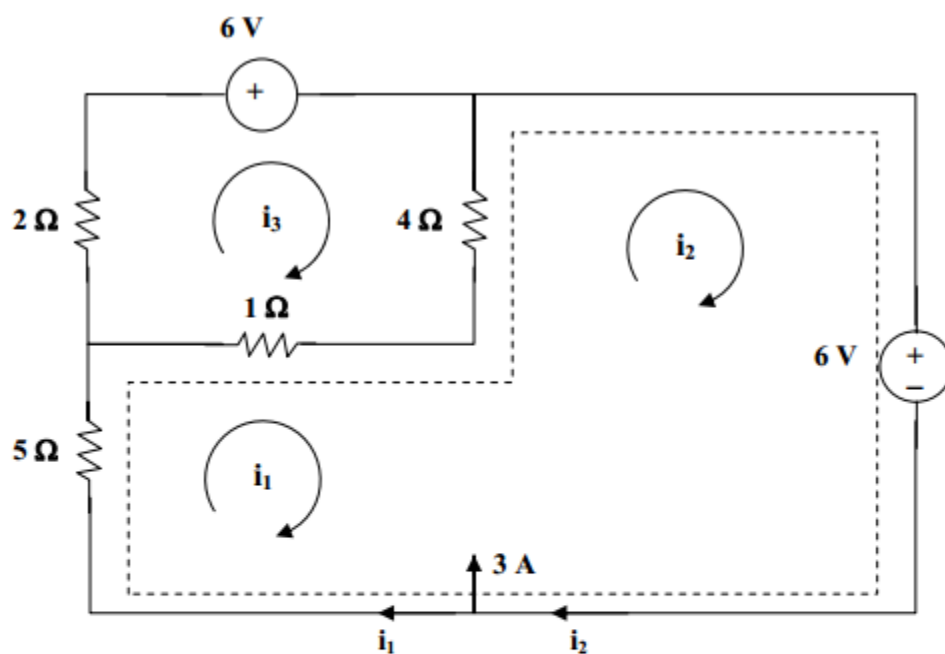
$$v_1 = \underline{4.97V}, \quad v_2 = \underline{4.85V}, \quad v_3 = \underline{-0.12V}.$$



Loop 1 and 2 form a supermesh. For the supermesh,


$$6i_1 + 4i_2 - 5i_3 + 12 = 0 \quad (1)$$

For loop 3,  $-i_1 - 4i_2 + 7i_3 + 6 = 0 \quad (2)$

Also,  $i_2 = 3 + i_1 \quad (3)$

Solving (1) to (3),  $i_1 = -3.067$ ,  $i_3 = -1.3333$ ;  $i_o = i_1 - i_3 = \underline{\underline{-1.7333 \text{ A}}}$


Voltage source acting alone:

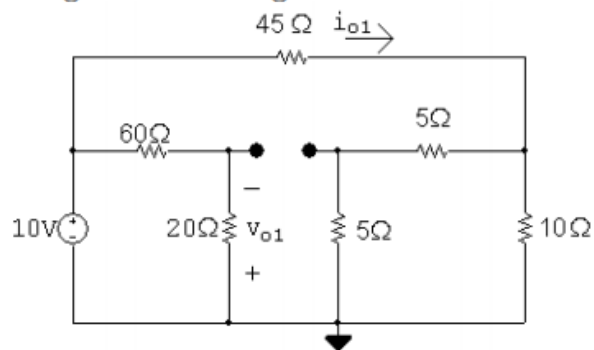

$$i_{o1} = \frac{10}{45 + (5 + 5) \parallel 10} = \frac{10}{45 + 5} = 0.2 \text{ A}$$

$$v_{o1} = \frac{20}{20 + 60}(-10) = -2.5 \text{ V}$$

Current source acting alone:

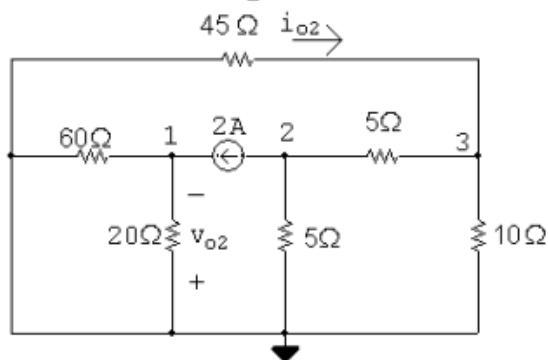

$$\frac{v_2}{5} + 2 + \frac{v_2 - v_3}{5} = 0$$

$$\frac{v_3}{10} + \frac{v_3 - v_2}{5} + \frac{v_3}{45} = 0$$

Solving,  $v_2 = -7.25 \text{ V} = v_{o2}$ ;  $v_3 = -4.5 \text{ V}$

$$i_{o2} = -\frac{v_3}{45} = -0.1 \text{ A}$$

$$i_{20} = \frac{60 \parallel 20}{20}(2) = 1.5 \text{ A}$$


$$v_{o2} = -20i_{20} = -20(1.5) = -30 \text{ V}$$

$$\therefore v_o = v_{o1} + v_{o2} = -2.5 - 30 = -32.5 \text{ V}$$

$$i_o = i_{o1} + i_{o2} = 0.2 + 0.1 = 0.3 \text{ A}$$

- [a] The mesh-current method does not directly involve the voltage drop across the 40 mA source. Instead, use the node-voltage method and choose the reference node so that a node voltage is identical to the voltage across the 40 mA source.

[b]

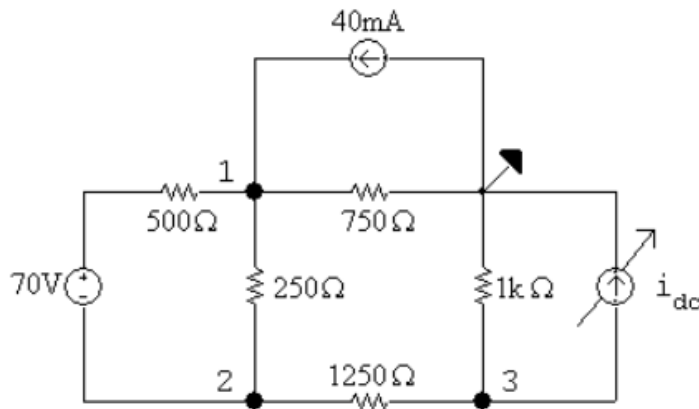

Since the 40 mA source is developing 0 W,  $v_1$  must be 0 V.

Since  $v_1$  is known, we can sum the currents away from node 1 to find  $v_2$  thus:

$$\frac{0 - (70 + v_2)}{500} + \frac{0 - v_2}{250} + \frac{0}{750} - 0.04 = 0$$

$$\therefore v_2 = -30 \text{ V}$$

Now that we know  $v_2$  we sum the currents away from node 2 to find  $v_3$ ; thus:

$$\frac{v_2 + 70 - 0}{500} + \frac{v_2 - 0}{250} + \frac{v_2 - v_3}{1250} = 0$$

$$\therefore v_3 = -80 \text{ V}$$

Now that we know  $v_3$  we sum the currents away from node 3 to find  $i_{dc}$ ; thus:

$$\frac{v_3}{1000} + \frac{v_3 - v_2}{1250} + i_{dc} = 0$$

$$\therefore i_{dc} = 0.12 = 120 \text{ mA}$$