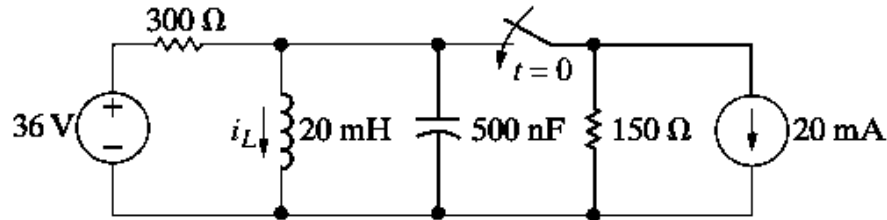



## Homwork 5 جواب سوالات

-۲



$$t < 0: \quad i_L(0^-) = \frac{36}{300} = 0.12 \text{ A}; \quad v_C(0^-) = 0 \text{ V}$$

The circuit reduces to:

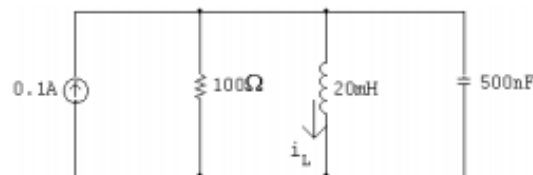

$$i_L(\infty) = 0.1 \text{ A}$$

$$\omega_o = \sqrt{\frac{1}{LC}} = \sqrt{\frac{1}{(20 \times 10^{-3})(500 \times 10^{-9})}} = 10,000 \text{ rad/s}$$

$$\alpha = \frac{1}{2RC} = \frac{1}{(100)(500 \times 10^{-9})} = 10,000 \text{ rad/s}$$

Critically damped:

$$i_L = 0.1 + D'_1 t e^{-10,000t} + D'_2 e^{-10,000t}$$

$$i_L(0) = 0.1 + D'_2 = 0.12 \quad \text{so} \quad D'_2 = 0.02$$

$$\frac{di_L}{dt}(0) = D'_1 - \alpha D'_2 = \frac{V_0}{L} \quad \text{so} \quad D'_1 - (10,000)(0.02) = 0$$


$$\text{Solving,} \quad D'_1 = 200$$

$$i_L(t) = 0.1 + 200t e^{-10,000t} + 0.02 e^{-10,000t} \text{ A}, \quad t \geq 0$$

$$\frac{dv_c}{dt}(0^+) = \frac{1}{C} i_c(0^+)$$

$$\frac{di_L}{dt}(0^+) = \frac{1}{L} V_L(0^+)$$


in  $t = 0^-$

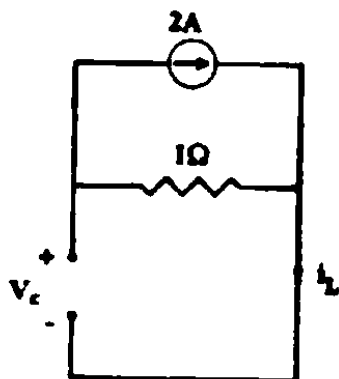

$$i_L(0) = 0$$

$$V_c(0) = -2$$


in  $t = 0^+$

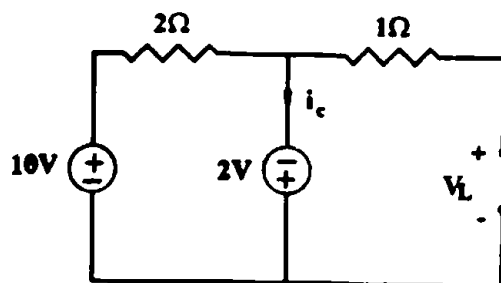

$$\begin{aligned} v_L(0^+) &= -2V \\ i_c(0^+) &= 6A \end{aligned} \Rightarrow \begin{cases} \frac{dv_c(0^+)}{dt} = 1 \times 6 = 6 \\ \frac{di_L(0^+)}{dt} = \frac{1}{1} \times -2 = -2 \end{cases}$$

For  $t < 0$ ,  $i(0) = 0$  and  $v(0) = 0$ .

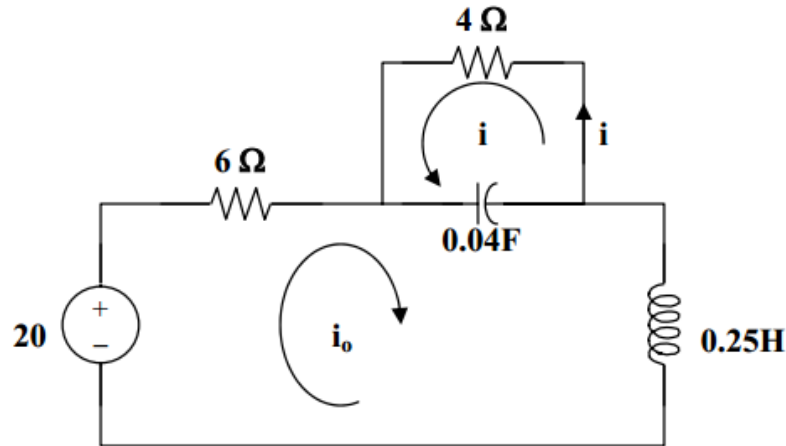For  $t > 0$ , the circuit is as shown below.



Applying KVL to the larger loop,

$$-20 + 6i_o + 0.25di_o/dt + 25 \int (i_o + i)dt = 0 \quad (1)$$

For the smaller loop,  $4i + 25 \int (i + i_o)dt = 0$  or  $\int (i + i_o)dt = -0.16i$  (2)

Taking the derivative,  $4di/dt + 25(i + i_o) = 0$  or  $i_o = -0.16di/dt - i$  (3)

and  $di_o/dt = -0.16d^2i/dt^2 - di/dt$  (4)

From (1), (2), (3), and (4),  $-20 - 0.96di/dt - 6i - 0.04d^2i/dt^2 - 0.25di/dt - 4i = 0$

Which becomes,  $d^2i/dt^2 + 30.25di/dt + 250i = -500$

This leads to,  $s^2 + 30.25s + 250 = 0$

$$\text{or } s_{1,2} = \frac{-30.25 \pm \sqrt{(30.25)^2 - 1000}}{2} = -15.125 \pm j4.608$$

This is clearly an underdamped response.

Thus,  $i(t) = I_s + e^{-15.125t}(A_1 \cos(4.608t) + A_2 \sin(4.608t))A$ .


At  $t = 0$ ,  $i_o(0) = 0$  and  $i(0) = 0 = I_s + A_1$  or  $A_1 = -I_s$ . As  $t$  approaches infinity,  $i_o(\infty) = 20/10 = 2A = -i(\infty)$  or  $i(\infty) = -2A = I_s$  and  $A_1 = 2$ .

In addition, from (3), we get  $di(0)/dt = -6.25i_o(0) - 6.25i(0) = 0$ .

$di/dt = 0 - 15.125 e^{-15.125t}(A_1 \cos(4.608t) + A_2 \sin(4.608t)) + e^{-15.125t}(-A_1 4.608 \sin(4.608t) + A_2 4.608 \cos(4.608t))$ . At  $t=0$ ,  $di(0)/dt = 0 = -15.125A_1 + 4.608A_2 = -30.25 + 4.608A_2$  or  $A_2 = 30.25/4.608 = 6.565$ .

This leads to,
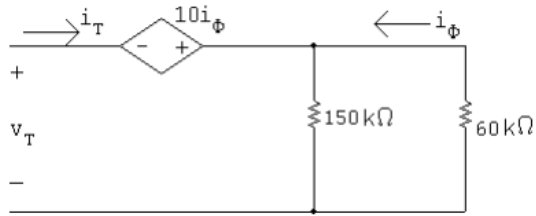
$$i(t) = \underline{(-2 + e^{-15.125t}(2\cos(4.608t) + 6.565\sin(4.608t)) A}$$



$$v_T = -10i_\phi + i_T \left( \frac{(150)(60)}{210} \right) = -10 \frac{-i_T(150)}{210} + i_T \frac{9000}{210}$$

$$\frac{v_T}{i_T} = \frac{1500 + 9000}{210} = 50\ \Omega$$

$$V_o = \frac{4000}{10,000}(50) = 20\text{ V}; \quad I_o = 0$$

$$i_C(0) = -i_R(0) - i_L(0) = -\frac{20}{50} = -0.4\text{ A}$$

$$\frac{i_C(0)}{C} = \frac{-0.4}{8 \times 10^{-6}} = -50,000$$

$$\omega_o = \sqrt{\frac{1}{LC}} = \sqrt{\frac{1}{(51.2 \times 10^{-3})(8 \times 10^{-6})}} = 1562.5\text{ rad/s}$$

$$\alpha = \frac{1}{2RC} = \frac{1}{(2)(50)(8 \times 10^{-6})} = 1250\text{ rad/s}$$

$$\alpha^2 < \omega_0^2 \quad \text{so the response is underdamped}$$

$$\omega_d = \sqrt{1562.5^2 - 1250^2} = 937.5$$


$$v_o = B_1 e^{-1250t} \cos 937.5t + B_2 e^{-1250t} \sin 937.5t$$

$$v_o(0) = B_1 20\text{ V}$$

$$\frac{dv_o}{dt}(0) = -\alpha B_1 + \omega_d B_2 = \frac{i_C(0)}{C}$$

$$\therefore \quad -1250(20) + 937.5 B_2 = -50,000 \quad \text{so} \quad B_2 = -26.67$$
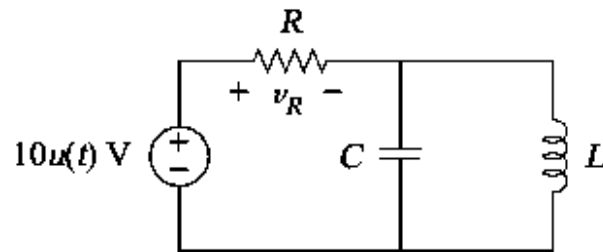
$$v_o = 20e^{-1250t} \cos 937.5t - 26.67e^{-1250t} \sin 937.5t\text{ V}, \quad t \geq 0$$



This is a parallel RLC circuit as evident when the voltage source is turned off.

$$\alpha = 1/(2RC) = (1)/(2 \times 3 \times (1/18)) = 3$$

$$\omega_o = 1/\sqrt{LC} = 1/\sqrt{2 \times 1/18} = 3$$

Since  $\alpha = \omega_o$ , we have a critically damped response.


$$s_{1,2} = -3$$

Let  $v(t)$  = capacitor voltage

Thus,  $v(t) = V_s + [(A + Bt)e^{-3t}]$  where  $V_s = 0$

$$\text{But } -10 + v_R + v = 0 \text{ or } v_R = 10 - v$$

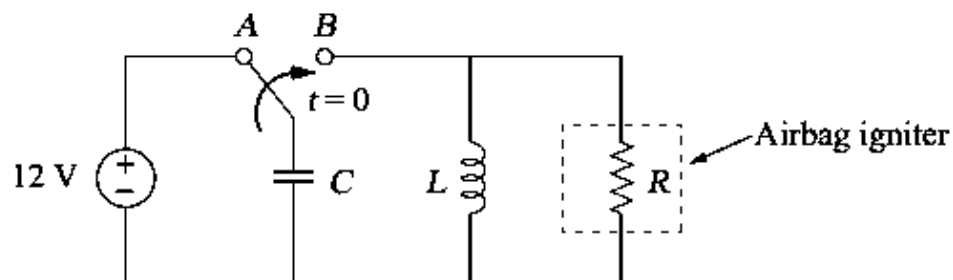Therefore  $v_R = \underline{10 - [(A + Bt)e^{-3t}]}$  where A and B are determined from initial conditions.



The voltage across the igniter is  $v_R = v_C$  since the circuit is a parallel RLC type.

$$v_C(0) = 12, \text{ and } i_L(0) = 0.$$

$$\alpha = 1/(2RC) = 1/(2 \times 3 \times 1/30) = 5$$

$$\omega_o = 1/\sqrt{LC} = 1/\sqrt{60 \times 10^{-3} \times 1/30} = 22.36$$

$\alpha < \omega_o$  produces an underdamped response.

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_o^2} = -5 \pm j21.794$$

$$v_C(t) = e^{-5t}(A \cos 21.794t + B \sin 21.794t) \quad (1)$$

$$v_C(0) = 12 = A$$

$$dv_C/dt = -5[(A \cos 21.794t + B \sin 21.794t)e^{-5t}]$$

$$+ 21.794[-A\sin 21.794t + B\cos 21.794t]e^{-5t} \quad (2)$$

$$dv_C(0)/dt = -5A + 21.794B$$

But,  $dv_C(0)/dt = -[v_C(0) + Ri_L(0)]/(RC) = -(12 + 0)/(1/10) = -120$

Hence,  $-120 = -5A + 21.794B$ , leads to  $B = (5 \times 12 - 120)/21.794 = -2.753$

At the peak value,  $dv_C(t_0)/dt = 0$ , i.e.,

$$0 = A + B\tan 21.794t_0 + (A21.794/5)\tan 21.794t_0 - 21.794B/5$$

$$(B + A21.794/5)\tan 21.794t_0 = (21.794B/5) - A$$

$$\tan 21.794t_0 = [(21.794B/5) - A]/(B + A21.794/5) = -24/49.55 = -0.484$$

Therefore,  $21.794t_0 = |-0.451|$

$$t_0 = |-0.451|/21.794 = \underline{\underline{20.68 \text{ ms}}}$$